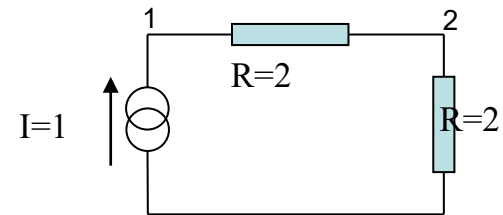


IR Drop: Solving Resistive Networks

- Can you solve the circuit at right?

- A more systematic way:

- Write circuit equation as $G \mathbf{V} = \mathbf{J}$
 - G is an $n \times n$ conductance matrix
 - \mathbf{V} is an $n \times 1$ vector of node voltages
 - \mathbf{J} is an $n \times 1$ vector of excitations
- Need to choose a ground node
- Can build the equations by inspection



Nodal Analysis

■ “Stamps”


- Conductance [1/resistor]: LHS only
- Current source: RHS only

$$G \mathbf{V} = \mathbf{J}$$

$$\begin{matrix} n1 \\ n2 \end{matrix} \begin{bmatrix} .. & +g & .. & -g & .. \\ .. & .. & .. & .. & .. \\ .. & -g & .. & +g & .. \\ .. & .. & .. & .. & .. \end{bmatrix}$$


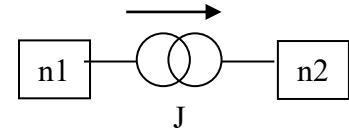
$$\begin{matrix} n1 \\ n2 \end{matrix} \begin{bmatrix} .. & .. & .. & .. \\ .. & .. & .. & .. \\ .. & .. & .. & .. \\ .. & .. & .. & .. \end{bmatrix} \begin{bmatrix} : \\ : \\ : \\ : \end{bmatrix} = \begin{bmatrix} -J \\ +J \end{bmatrix}$$




- For every such branch in the circuit, superpose the contributions
 - (Can also build stamps for other elements, extend to general circuits – basically, that’s how SPICE works)

Modified Nodal Analysis

■ “Stamps”

- Voltage source: Both sides additional rows and columns


- $G \mathbf{V} = \mathbf{J}$

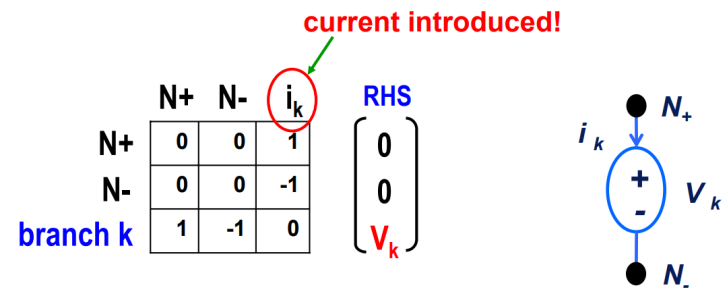

■ For every such branch in the circuit, superpose the contributions

- (Can also build stamps for other elements, extend to general circuits
 - basically, that's how SPICE works)

IR Drop: Back to the circuit

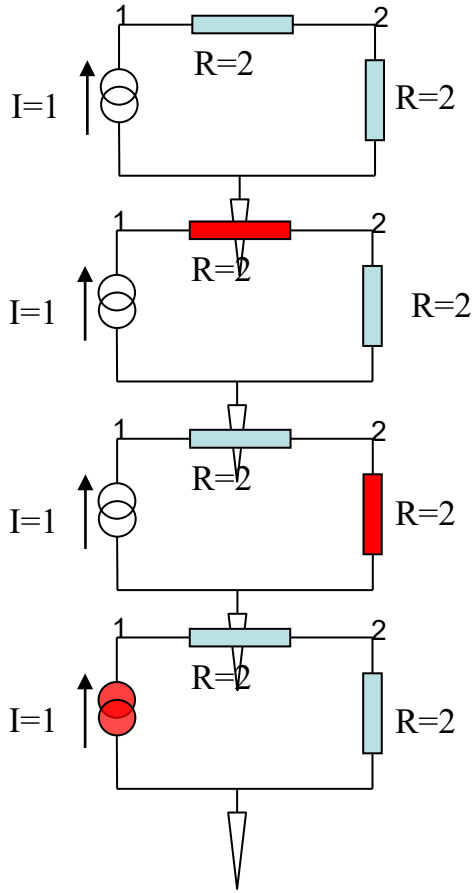


$$\begin{bmatrix} 0 & 0 \\ 0 & 0 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \end{bmatrix}$$

$$\begin{bmatrix} 0.5 & -0.5 \\ -0.5 & 0.5 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \end{bmatrix}$$

$$\begin{bmatrix} 0.5 & -0.5 \\ -0.5 & 1.0 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \end{bmatrix}$$

$$\begin{bmatrix} 0.5 & -0.5 \\ -0.5 & 1.0 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 1 \\ 0 \end{bmatrix}$$

$$\Rightarrow V_1 = 4 \quad V_2 = 2$$

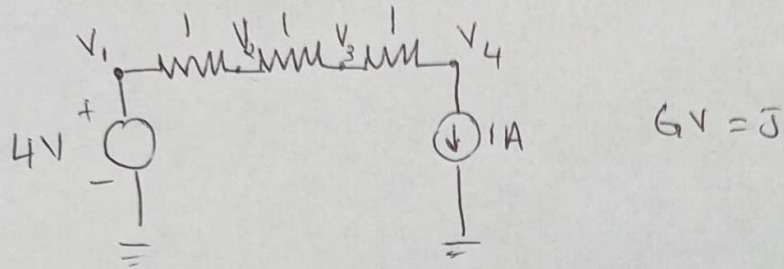


stamp in ~~all~~ element stamps into $GV = J$ system of equations.

$$\begin{array}{c}
 n_1 \\
 n_2 \\
 n_3 \\
 n_4 \\
 b
 \end{array}
 \begin{bmatrix}
 n_1 & n_2 & n_3 & n_4 & b \\
 +1 & -1 & 0 & 0 & +1 \\
 -1 & +1+1 & -1 & 0 & 0 \\
 0 & -1 & +1+1 & -1 & 0 \\
 0 & 0 & -1 & +1 & 0 \\
 +1 & 0 & 0 & 0 & 0
 \end{bmatrix}
 \begin{bmatrix}
 V_1 \\
 V_2 \\
 V_3 \\
 V_4 \\
 i_b
 \end{bmatrix}
 =
 \begin{bmatrix}
 0 \\
 0 \\
 0 \\
 -1 \\
 +4
 \end{bmatrix}$$

So now you can solve any resistive network (or thermal network)

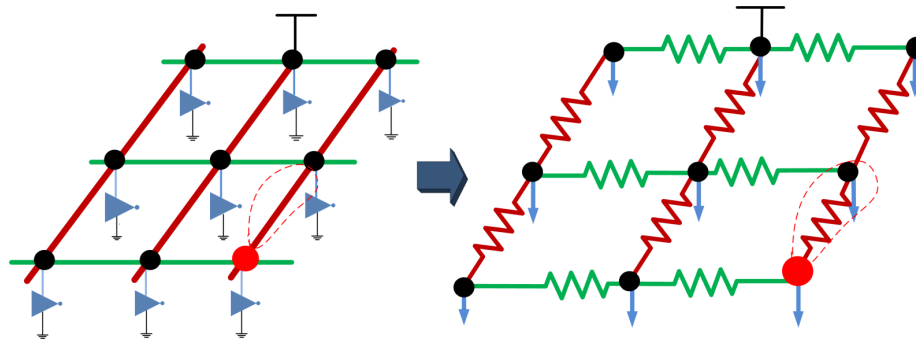- Network of resistors and current sources, some nodes at a fixed voltage



- Power grid analysis and thermal analysis use the same core technology)